



Welcome to PEEEB



Lecture 3: Diode Rectifiers

Presenter: Dr. Firuz Zare

www.peeeb.com

Contents:

Single phase half-wave diode rectifier

Single phase half-wave diode rectifier with freewheeling diode (R-L load)

Battery charger (with R or L component as a current limiter)

Single phase full wave diode rectifier with centre-tapped transformer

Single phase full wave diode rectifier (different loads)

Six-phase diode rectifier

Three-phase diode rectifier

Three-phase full-wave diode rectifier


Line impedance effects

Examples

Presenter: Dr. Firuz Zare

www.peeeb.com



Uncontrolled AC to DC Converter

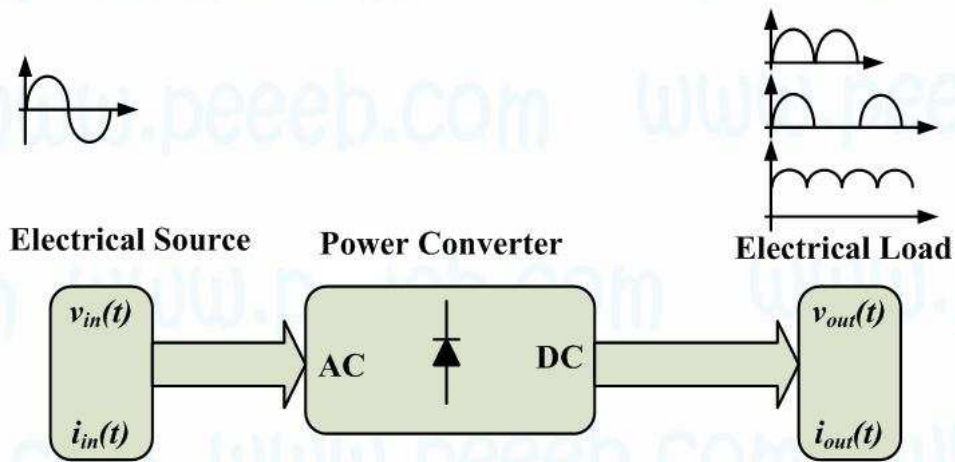

Presenter: Dr. Firuz Zare

www.peeeeb.com

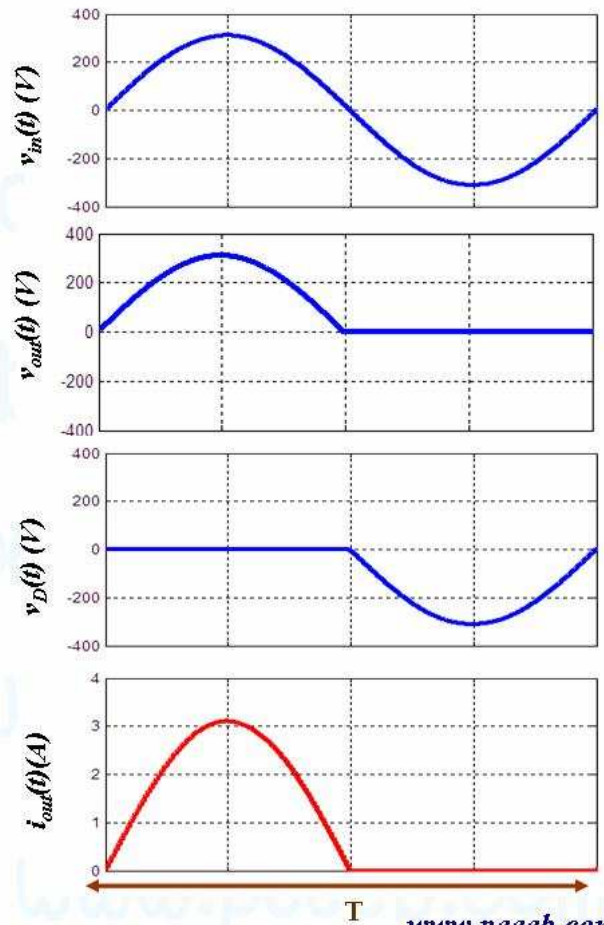
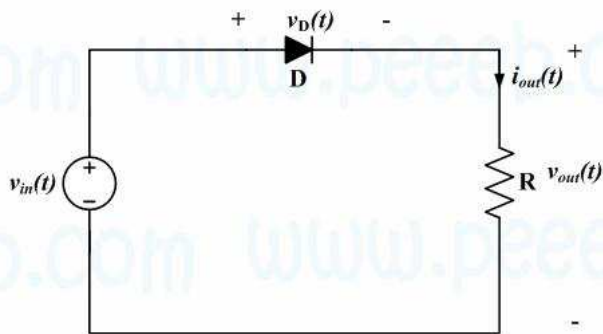
Single-phase half-wave diode-rectifier (resistive load)



Presenter: Dr. Firuz Zare

www.peeeb.com

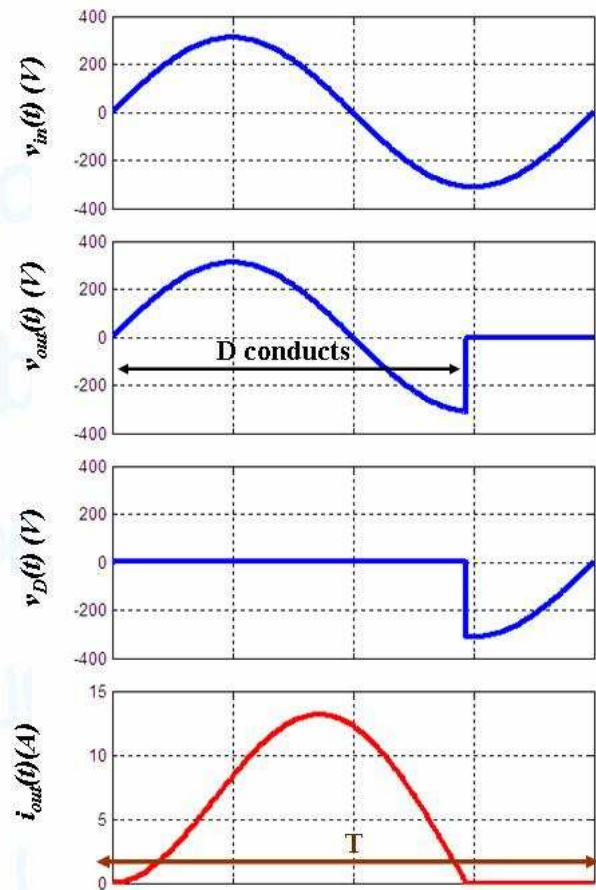
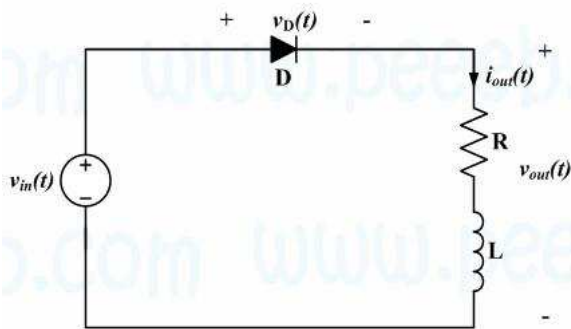
Single-phase half-wave diode-rectifier (resistive and inductive load)



Presenter: Dr. Firuz Zare

www.pееeb.com

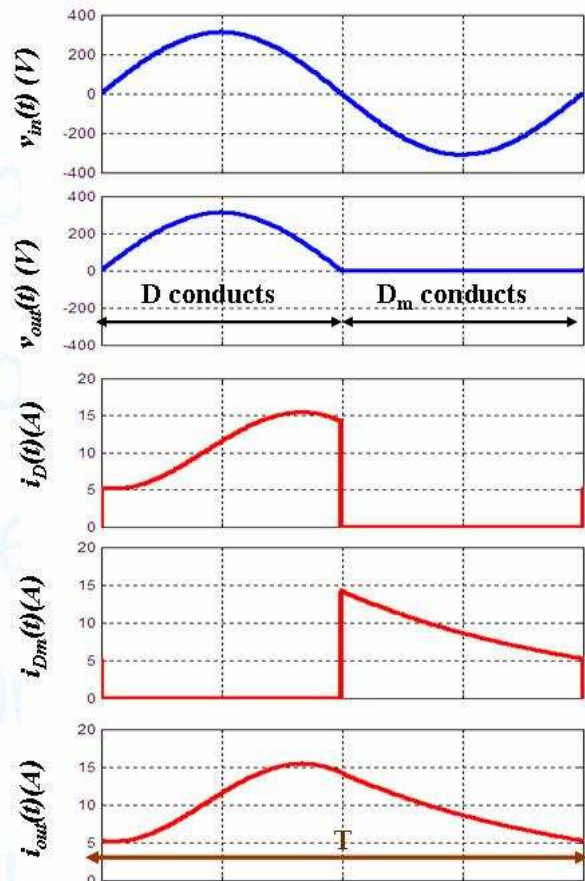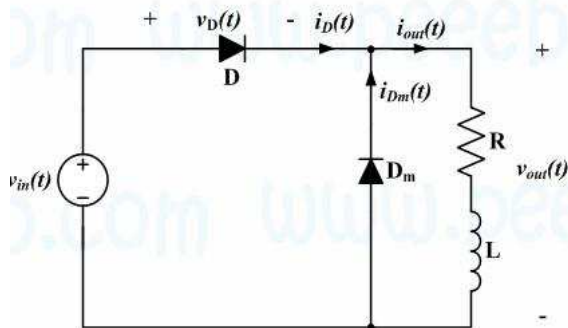Single-phase half-wave diode-rectifier with a freewheeling diode (resistive and inductive load)



Presenter: Dr. Firuz Zare

www.peeeb.com

Single-phase half-wave diode-rectifier

$$v_{out}(t) = \begin{cases} V_m \sin\left(\frac{2\pi t}{T}\right) & 0 < t \leq \frac{T}{2} \\ 0 & \frac{T}{2} < t \leq T \end{cases}$$

$$V_{out} = \overline{v_{out}(t)} = \frac{1}{T} \int_0^T v_{out}(t) dt$$


$$= \frac{1}{T} \int_0^{\frac{T}{2}} V_m \sin\left(\frac{2\pi t}{T}\right) dt + \frac{1}{T} \int_{\frac{T}{2}}^T 0 \times dt$$

$$= \frac{V_m}{T} \left(\frac{T}{2\pi} \right) \left[-\cos\left(\frac{2\pi t}{T}\right) \right]_0^{\frac{T}{2}}$$

$$= \frac{V_m}{2\pi} [-\cos(\pi) + \cos(0)]$$

$$= \frac{V_m}{2\pi} [-(-1) + 1]$$


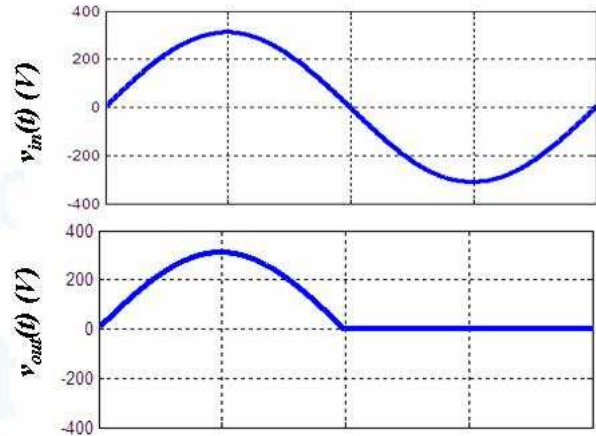
$$= \frac{V_m}{2\pi} [2] = \frac{V_m}{\pi}$$



Presenter: Dr. Firuz Zare

www.peeeb.com

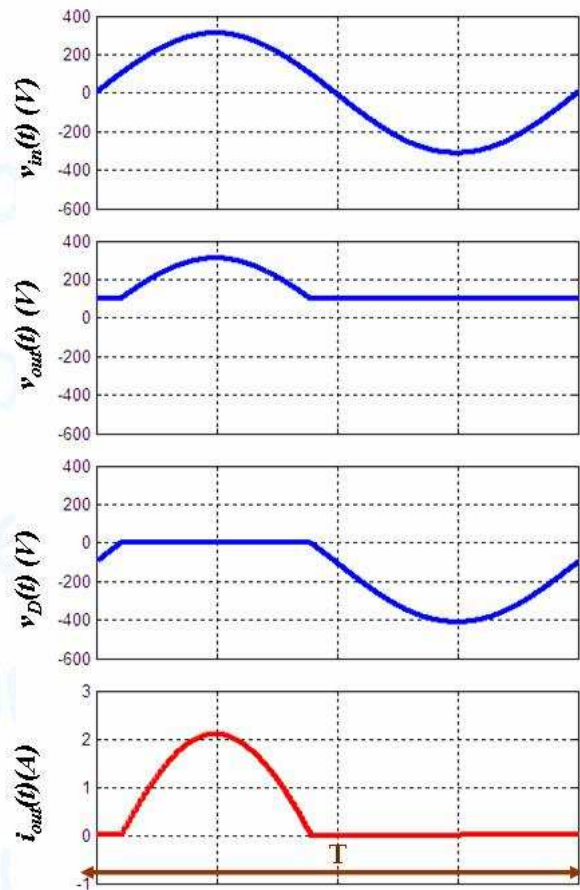
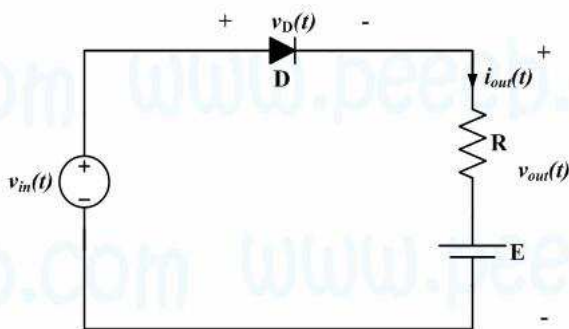
Single-phase half-wave battery charger with a resistor as a current limiter



Presenter: Dr. Firuz Zare

www.peeeb.com

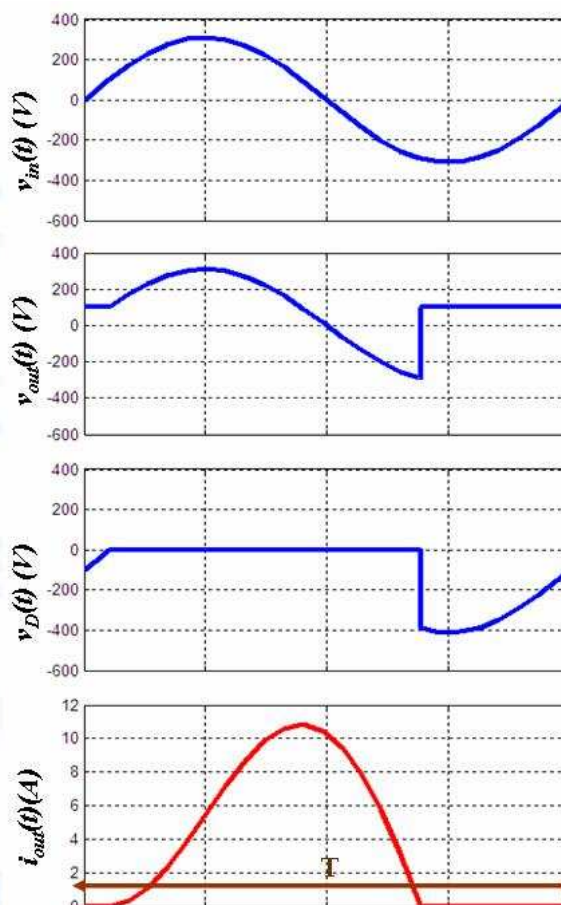
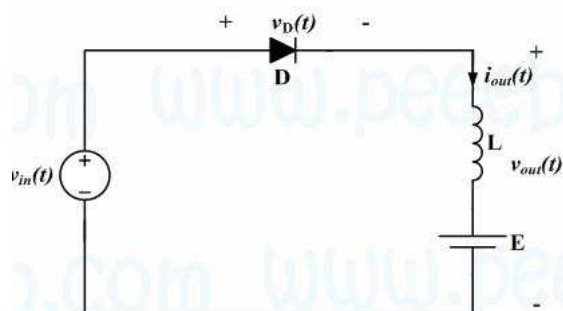
Single-phase half-wave battery charger with an inductor as a current limiter



Presenter: Dr. Firuz Zare

www.peeeb.com

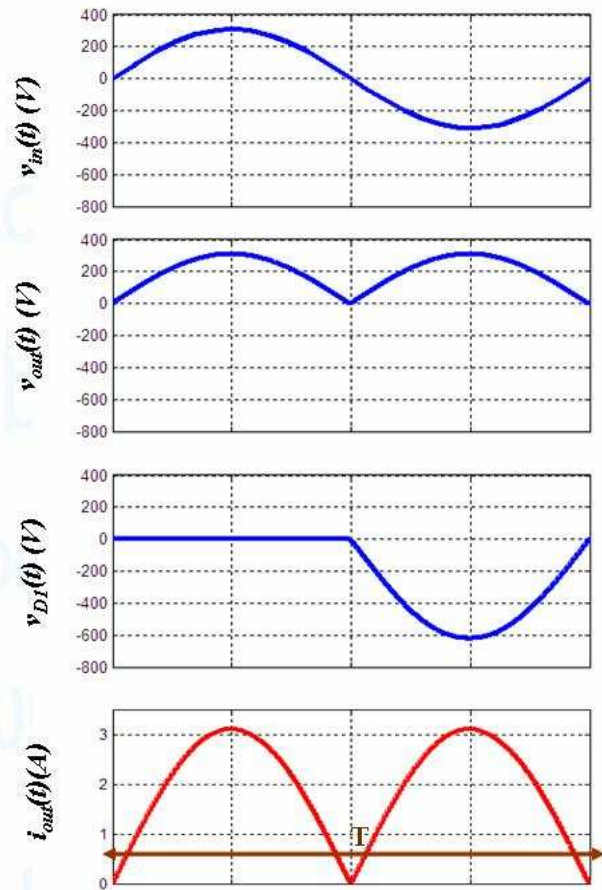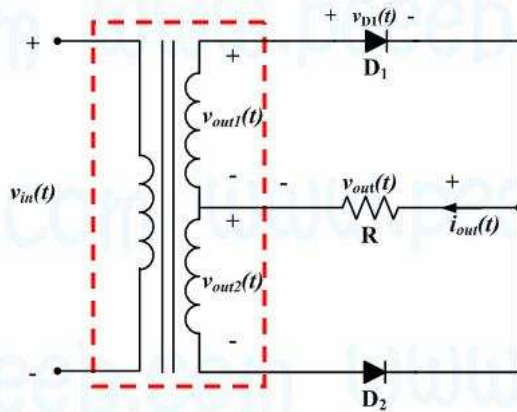
Single-phase full-wave diode rectifier with a centre-tapped transformer and a resistive load



Presenter: Dr. Firuz Zare

www.peeeb.com


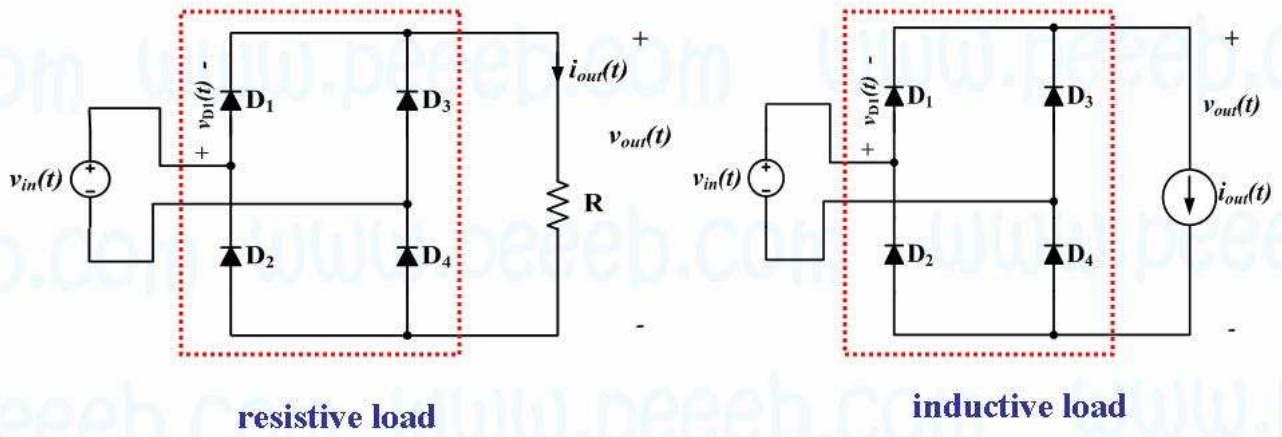
Single-phase full-wave diode rectifier (bridge rectifier)



Presenter: Dr. Firuz Zare

www.peeeb.com

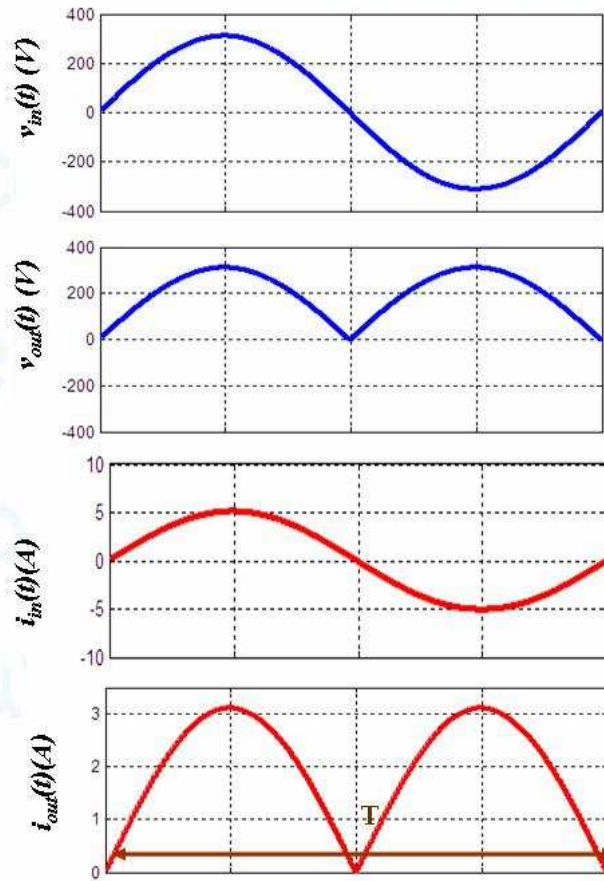
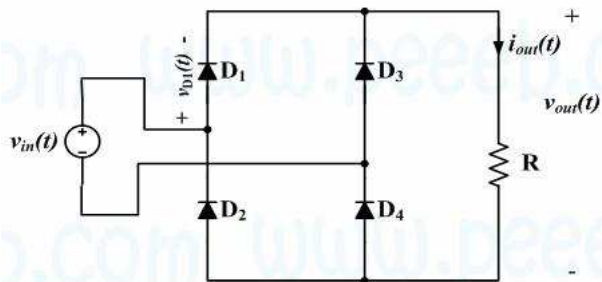
Single-phase full-wave diode rectifier with a resistive load



Presenter: Dr. Firuz Zare

www.peeeb.com

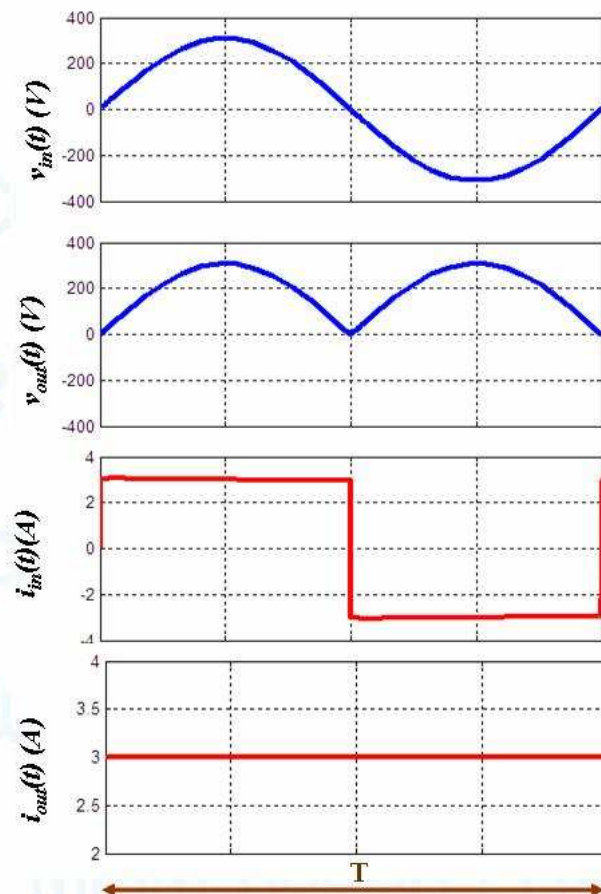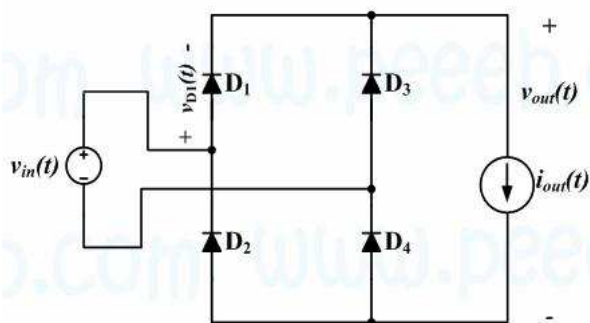Single-phase full-wave diode rectifier with an inductive load



Presenter: Dr. Firuz Zare

www.pееeb.com

Single-phase full-wave diode-rectifier


$$v_{out}(t) = \begin{cases} V_m \sin\left(\frac{2\pi t}{T}\right) & 0 < t \leq \frac{T}{2} \\ V_m \sin\left(\frac{2\pi t}{T}\right) & \frac{T}{2} < t \leq T \end{cases}$$

$$V_{out} = \overline{v_{out}(t)} = \frac{1}{T} \int_0^T v_{out}(t) dt$$

$$= \frac{1}{T} \int_0^{\frac{T}{2}} V_m \sin\left(\frac{2\pi t}{T}\right) dt + \frac{1}{T} \int_{\frac{T}{2}}^T V_m \sin\left(\frac{2\pi t}{T}\right) dt$$

$$= 2 \left(\frac{1}{T} \int_0^{\frac{T}{2}} V_m \sin\left(\frac{2\pi t}{T}\right) dt \right)$$


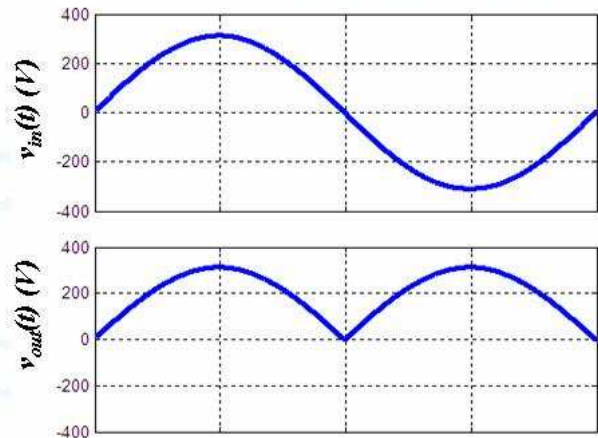
$$= 2 \left(\frac{V_m}{\pi} \right) = \frac{2V_m}{\pi}$$



Presenter: Dr. Firuz Zare

www.peeeb.com

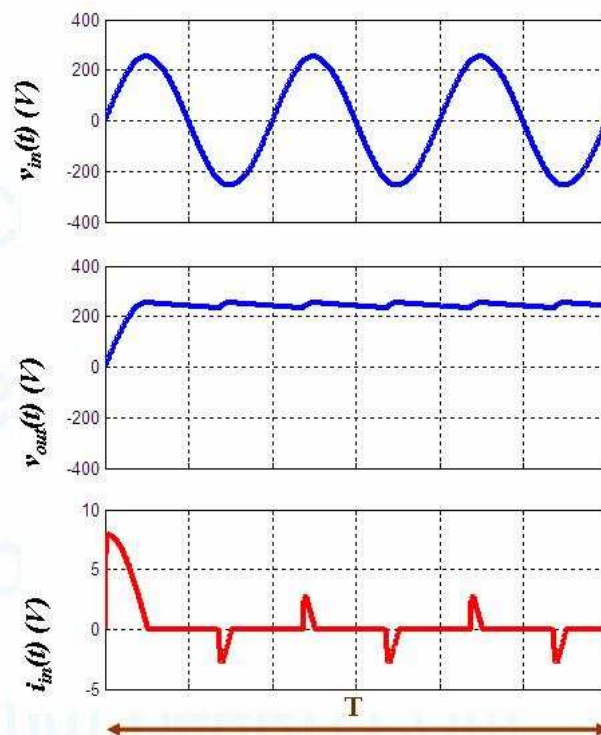
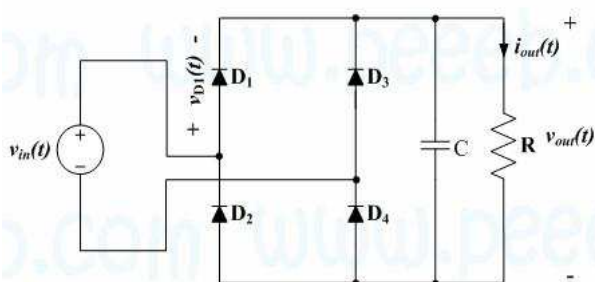
Single-phase full-wave diode rectifier as a DC power supply



Presenter: Dr. Firuz Zare

www.peeeb.com

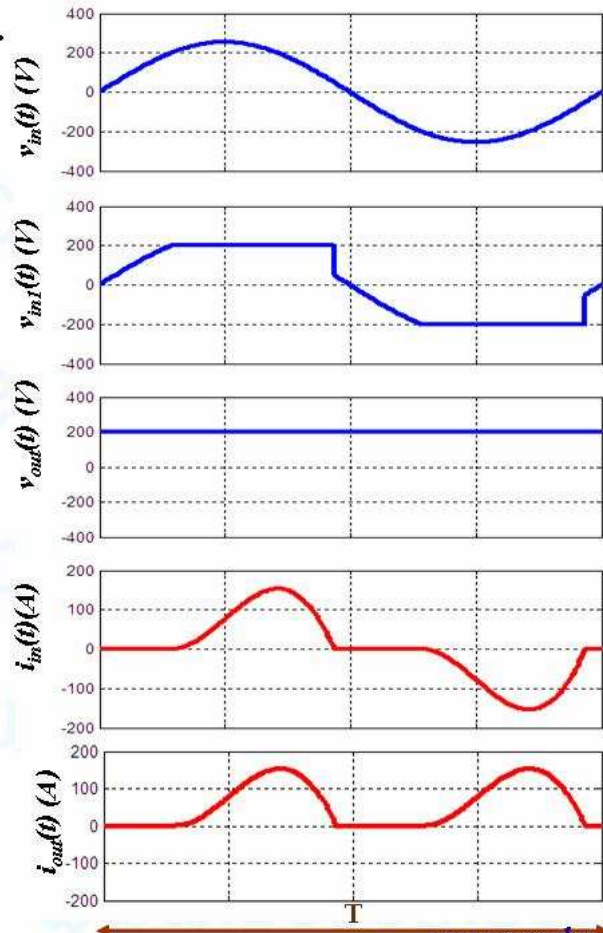
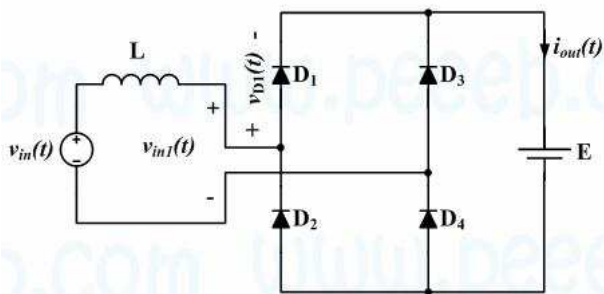
Single-phase full-wave battery charger with an inductor at the input side



Presenter: Dr. Firuz Zare

www.peeeeb.com

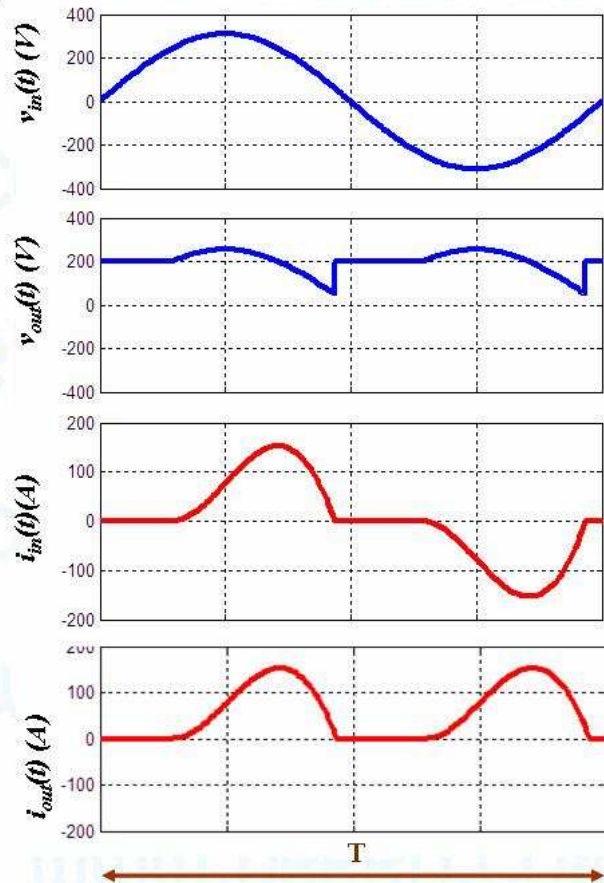
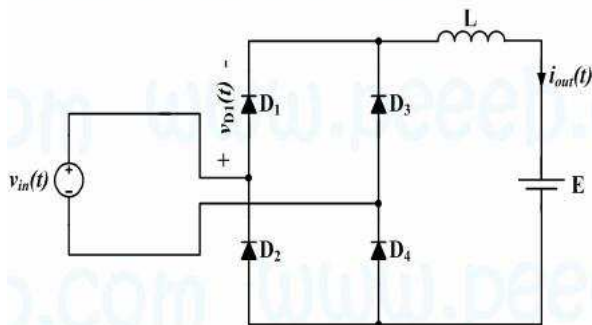
Single-phase full-wave battery charger with an inductor at the output side



Presenter: Dr. Firuz Zare

www.peeeeb.com

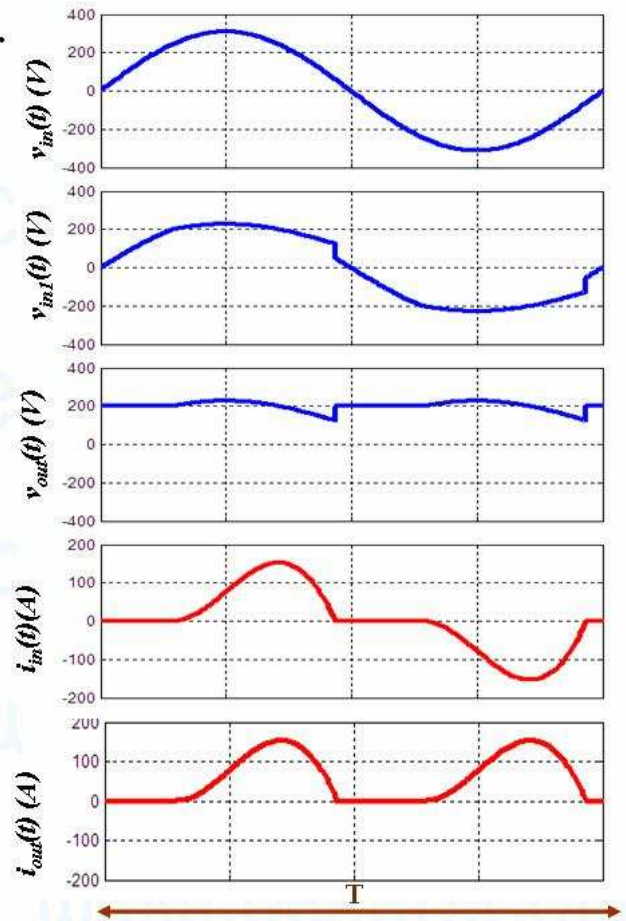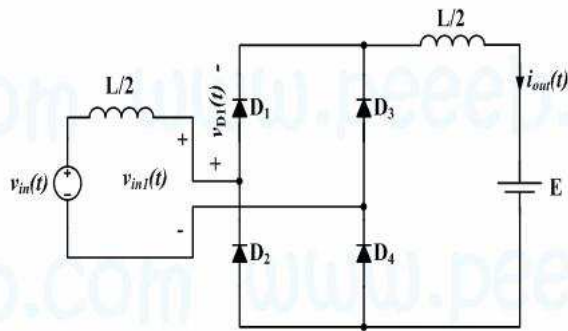
Single-phase full-wave battery charger with an inductor at the both sides




Presenter: Dr. Firuz Zare

www.peeeb.com

Doubling Output Voltage

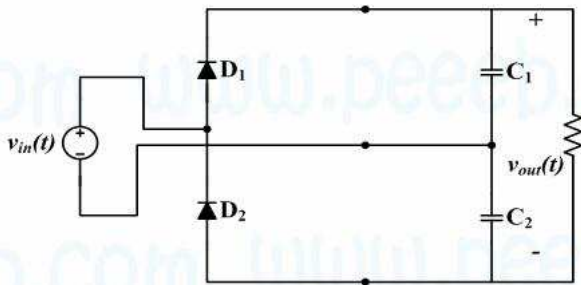


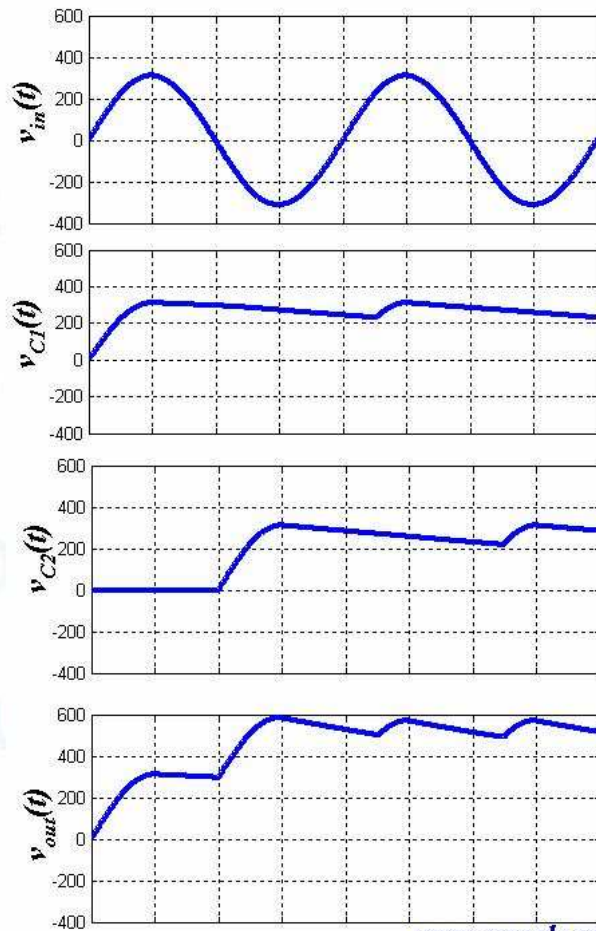
The capacitor C_1 is charged through the diode D_1 during the positive half-cycle of the input AC voltage and C_2 is charged through D_2 during the negative half-cycle.



Presenter: Dr. Firuz Zare

www.peeeb.com


Doubling Output Voltage

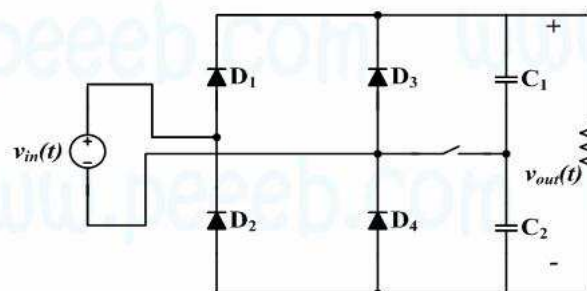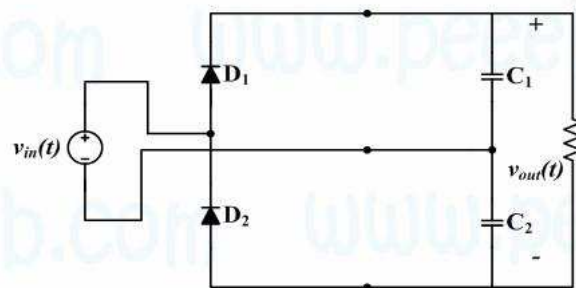


Presenter: Dr. Firuz Zare

www.peeeeb.com

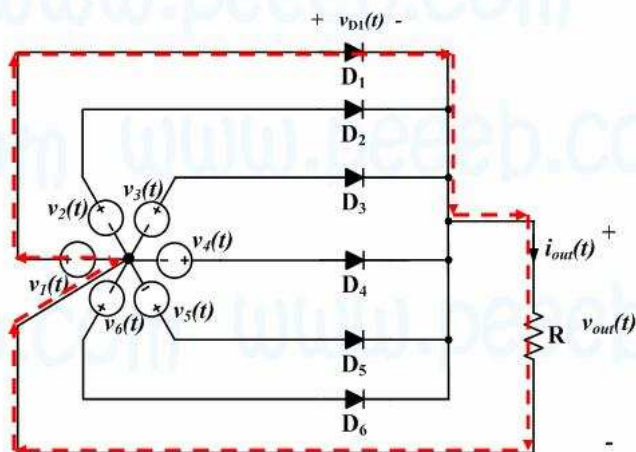Six-phase half-wave diode rectifier with star connection and resistive load



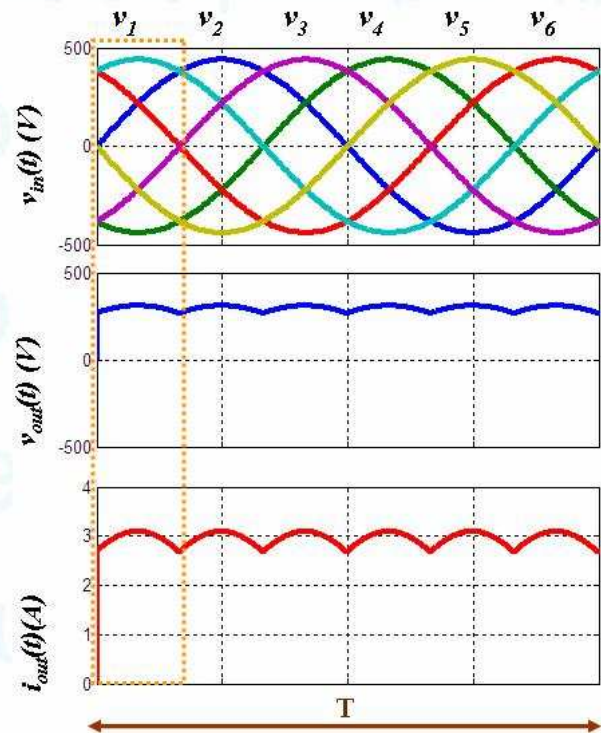
V_1 has the highest magnitude compare to other phases. Thus during this period D_1 conducts and the rest of diodes are reverse biased.




Presenter: Dr. Firuz Zare

www.peeeb.com

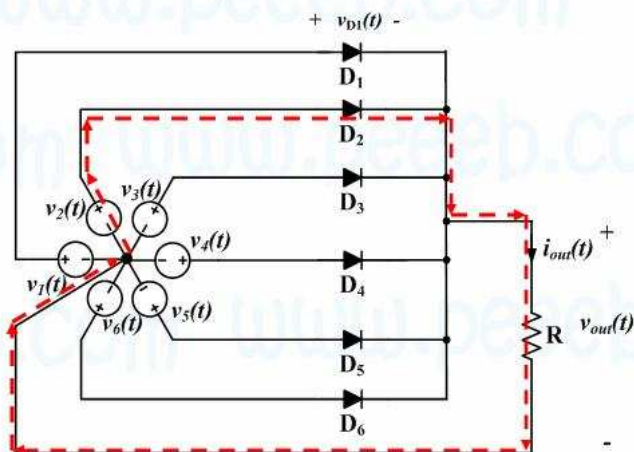Six-phase half-wave diode rectifier with star connection and resistive load



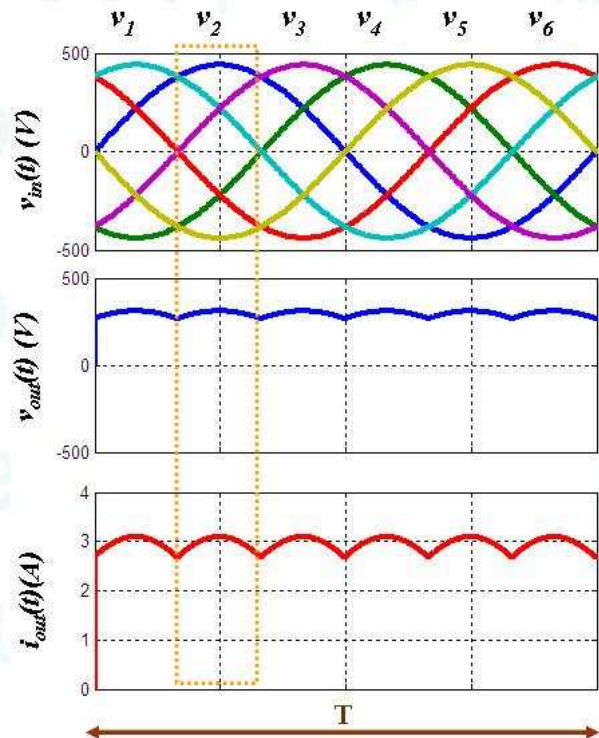
Now, $V_2 > V_1$ and other phases, thus during this period, D_1 is turned off and D_2 is turned on.




Presenter: Dr. Firuz Zare

www.peeeb.com

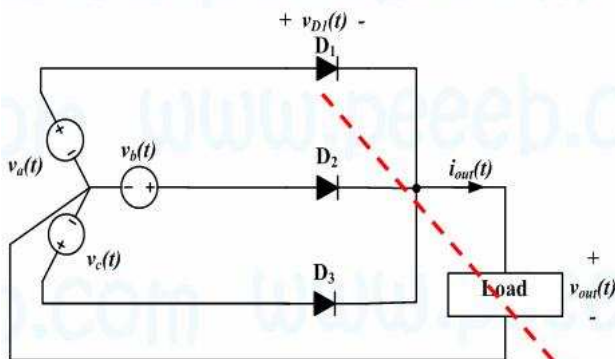Three-phase half-wave diode rectifier with star connection



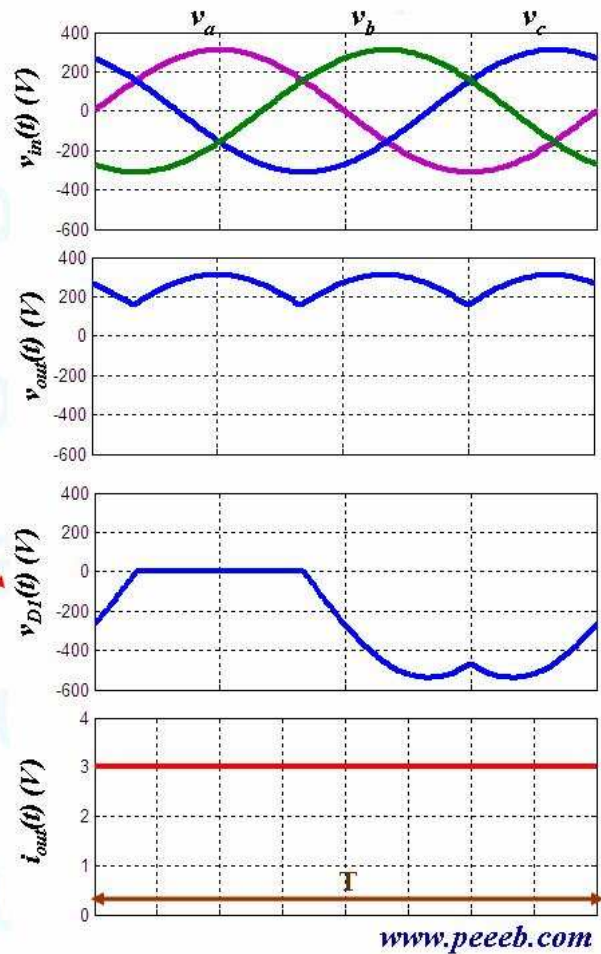When D_1 is off, $V_{D1} = V_a - V_b$ or $V_a - V_c$ which is a line voltage



Presenter: Dr. Firuz Zare

www.peeeb.com

Three-phase half-wave diode-rectifier

$$v_{out}(t) = V_m \cos\left(\frac{2\pi t}{T}\right) \quad -\frac{T}{6} < t \leq \frac{T}{6}$$


$$V_{out} = \frac{1}{3} \int_{-\frac{T}{6}}^{\frac{T}{6}} V_m \cos\left(\frac{2\pi t}{T}\right) dt$$

$$= \frac{3V_m}{T} \left(\frac{T}{2\pi} \right) \left[\sin\left(\frac{2\pi t}{T}\right) \right]_{-\frac{T}{6}}^{\frac{T}{6}}$$

$$= \frac{3V_m}{2\pi} \left[\sin\left(\frac{\pi}{3}\right) - \sin\left(-\frac{\pi}{3}\right) \right]$$

$$= \frac{3V_m}{2\pi} \left[\sin\left(\frac{\pi}{3}\right) + \sin\left(\frac{\pi}{3}\right) \right] = \frac{3V_m}{2\pi} \left[2 \sin\left(\frac{\pi}{3}\right) \right]$$

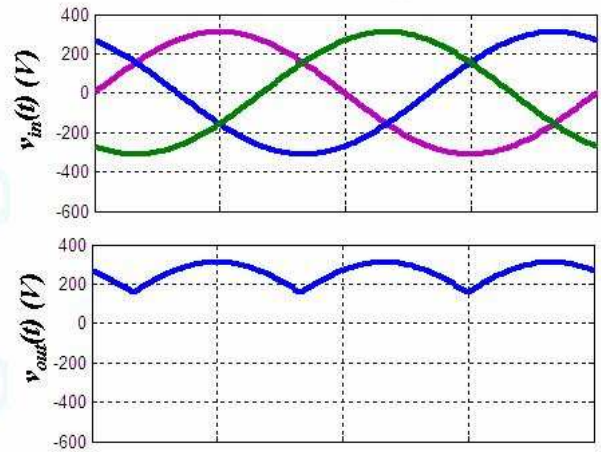
$$= \frac{3V_m}{\pi} \left[\frac{\sqrt{3}}{2} \right] = \frac{3\sqrt{3}V_m}{2\pi}$$






Presenter: Dr. Firuz Zare

www.peeeeb.com

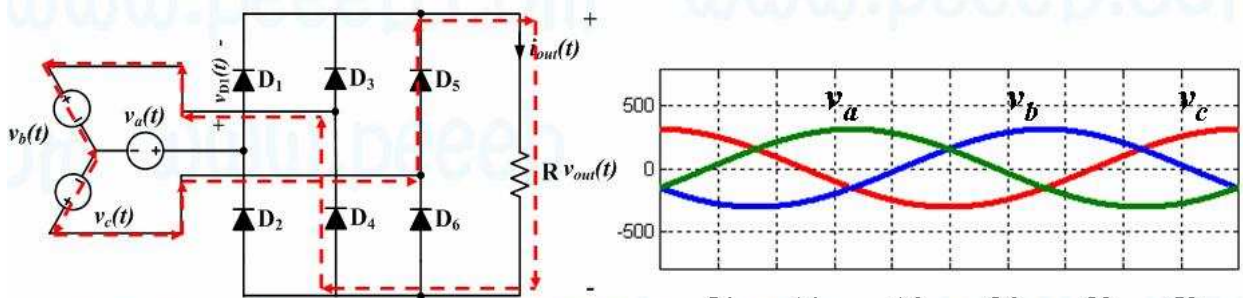Three-phase full-wave diode rectifier with resistive load





Diodes which are turned on

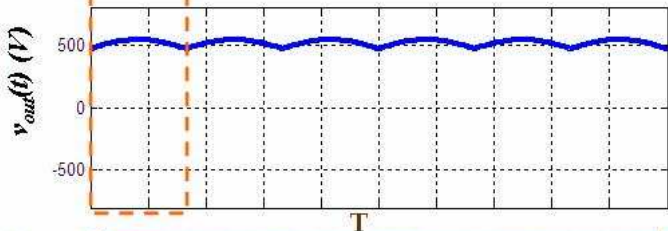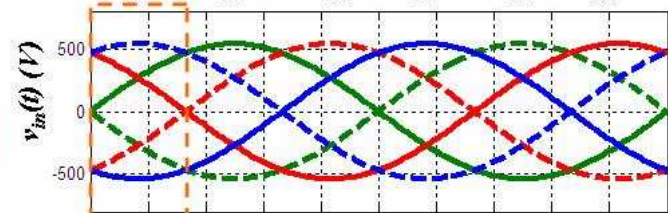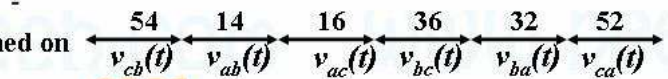




Presenter: Dr. Firuz Zare

www.pееeb.com

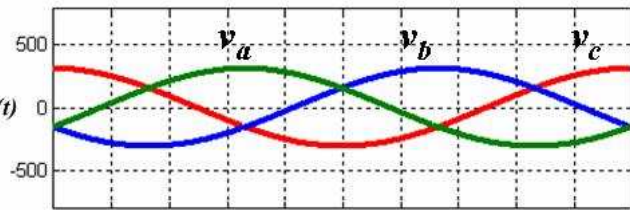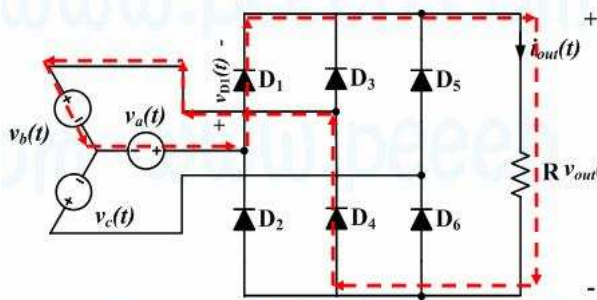Three-phase full-wave diode rectifier with resistive load



Diodes which are turned on

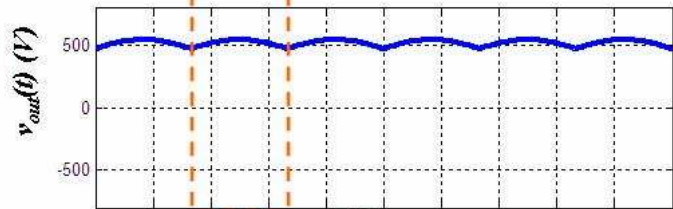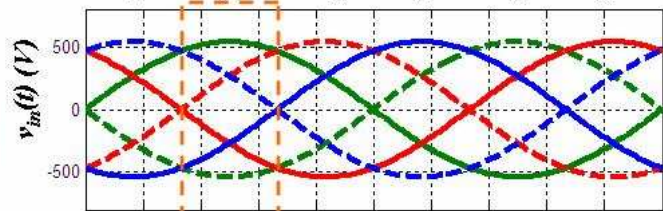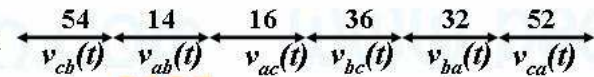


T




Presenter: Dr. Firuz Zare

www.peeeb.com

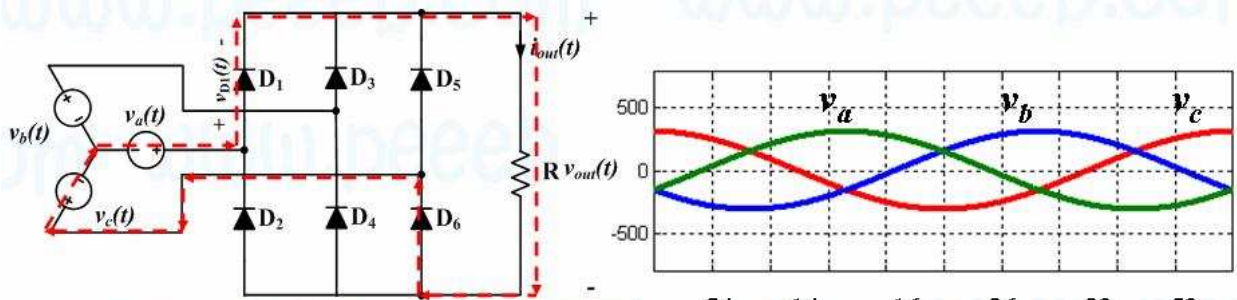Three-phase full-wave diode rectifier with resistive load



Diodes which are turned on

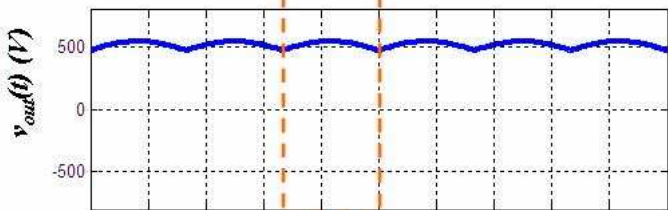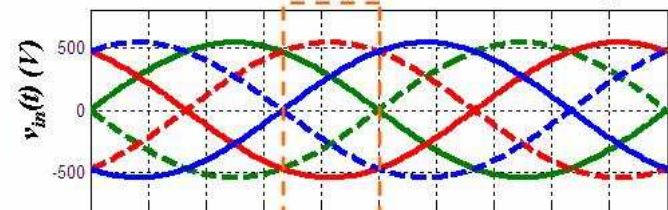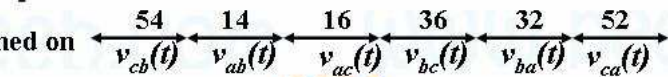


T




Presenter: Dr. Firuz Zare

www.peeeeb.com

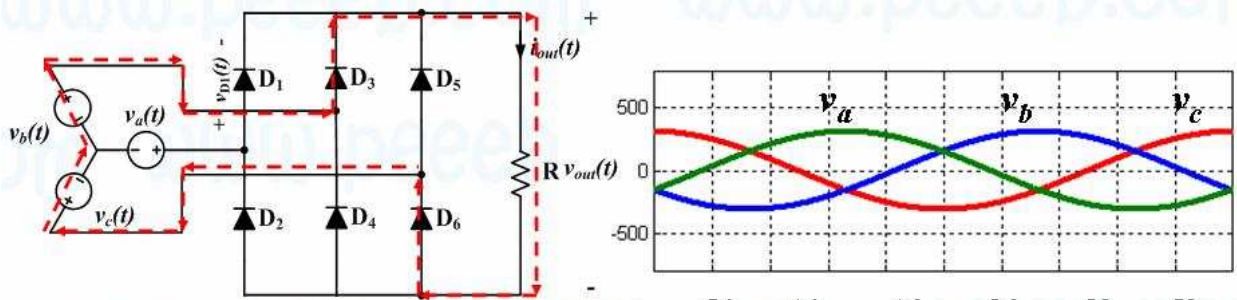Three-phase full-wave diode rectifier with resistive load



Diodes which are turned on

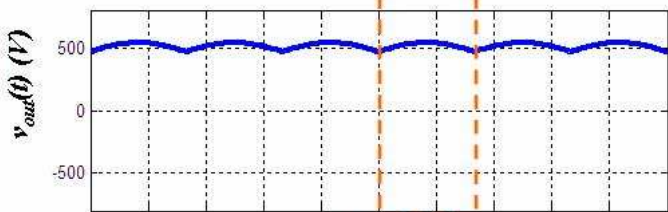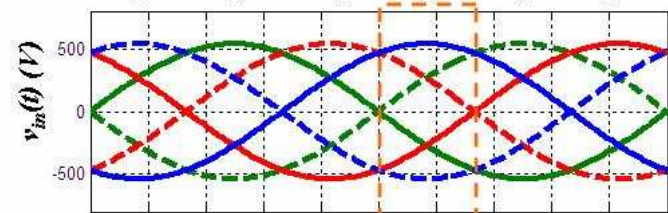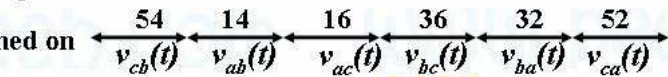


T




Presenter: Dr. Firuz Zare

www.peeeeb.com

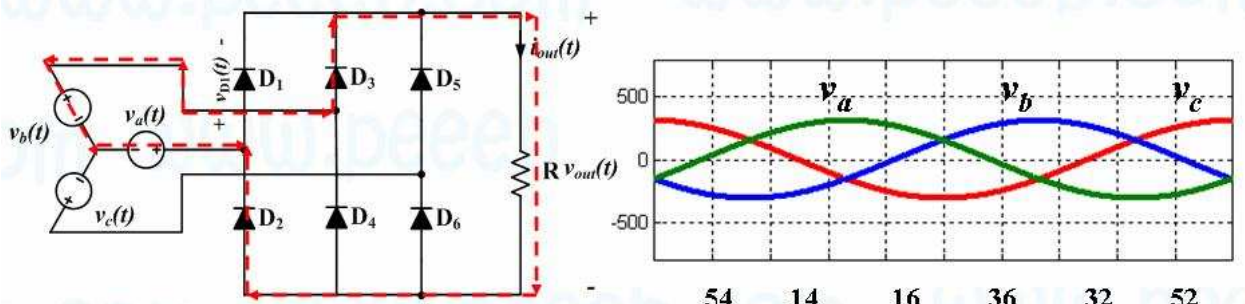Three-phase full-wave diode rectifier with resistive load



Diodes which are turned on

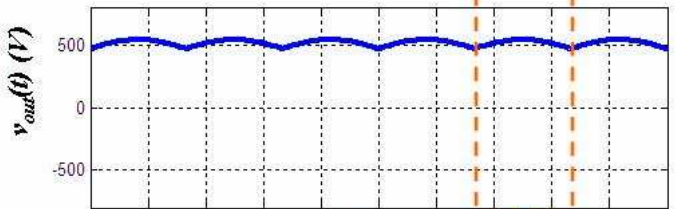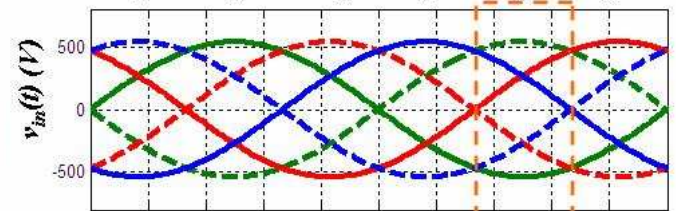
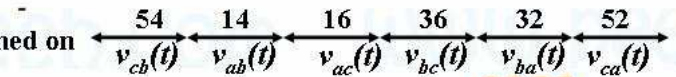


T




Presenter: Dr. Firuz Zare

www.peeeeb.com

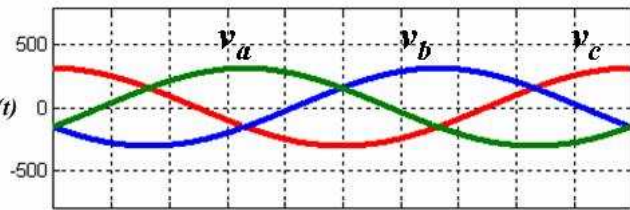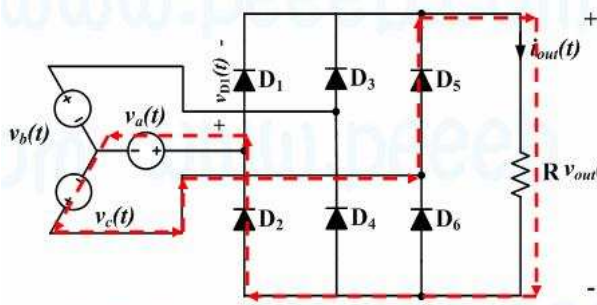Three-phase full-wave diode rectifier with resistive load




Diodes which are turned on

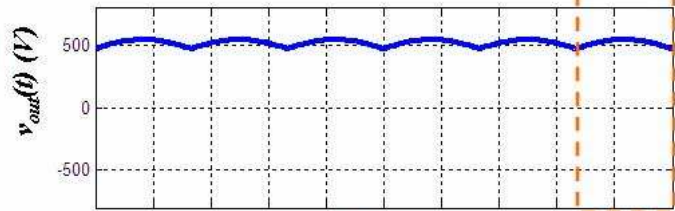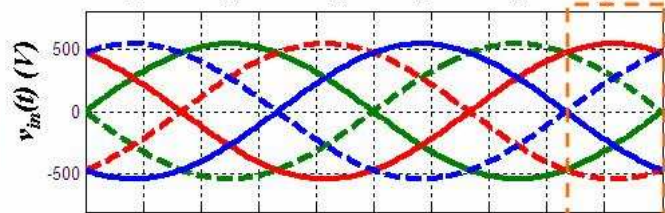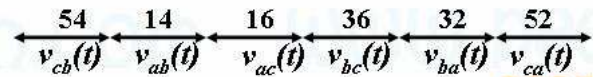

Presenter: Dr. Firuz Zare

www.peeeeb.com

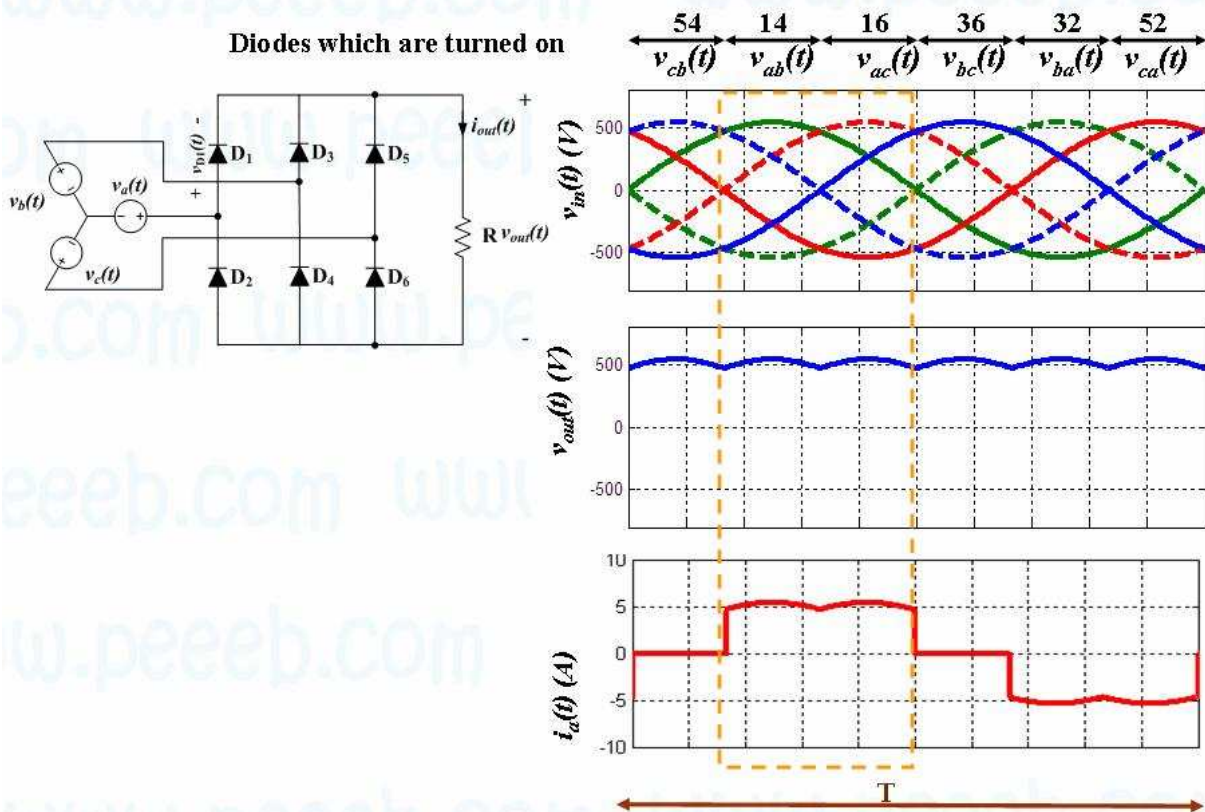Three-phase full-wave diode rectifier with resistive load





Presenter: Dr. Firuz Zare

www.peeeeb.com

Three-phase full-wave diode-rectifier

$$\begin{aligned}
 v_{out}(t) &= \sqrt{3}V_m \cos\left(\frac{2\pi t}{T}\right) \\
 V_{out} &= \frac{1}{T} \int_{-\frac{T}{12}}^{\frac{T}{12}} \sqrt{3}V_m \cos\left(\frac{2\pi t}{T}\right) dt \\
 &= \frac{6\sqrt{3}V_m}{T} \left(\frac{T}{2\pi}\right) \left[\sin\left(\frac{2\pi t}{T}\right) \right]_{-\frac{T}{12}}^{\frac{T}{12}} \\
 &= \frac{3\sqrt{3}V_m}{\pi} \left[\sin\left(\frac{\pi}{6}\right) - \sin\left(-\frac{\pi}{6}\right) \right] \\
 &= \frac{3\sqrt{3}V_m}{\pi} \left[\frac{1}{2} + \frac{1}{2} \right] = \frac{3\sqrt{3}V_m}{\pi}
 \end{aligned}$$



$$-\frac{T}{12} < t \leq \frac{T}{12}$$

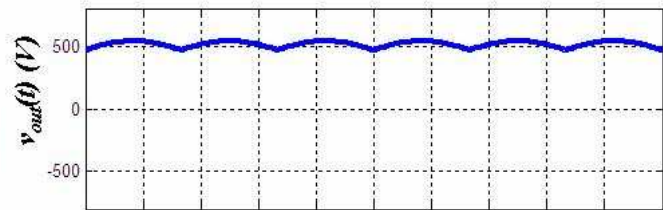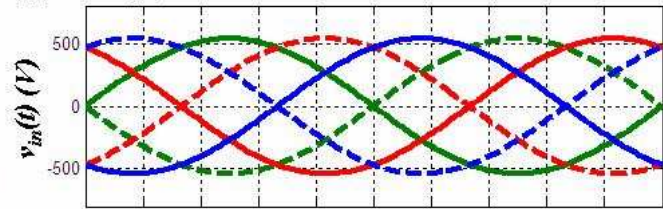

Presenter: Dr. Firuz Zare

www.peeeeb.com

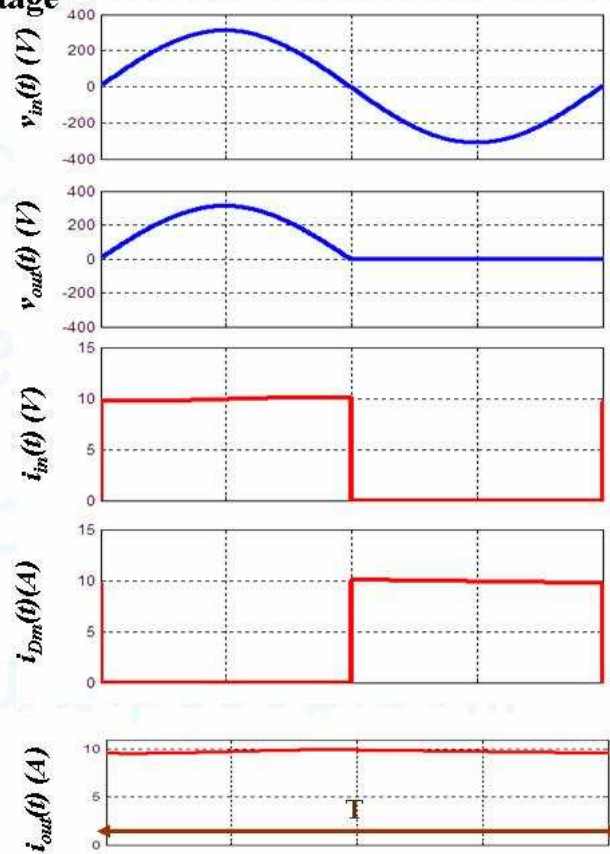
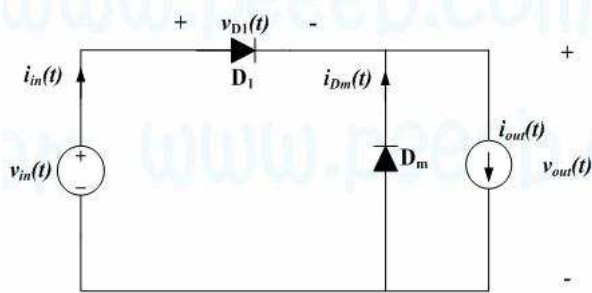
Effects of line impedance on output voltage



Presenter: Dr. Firuz Zare

www.peeeb.com

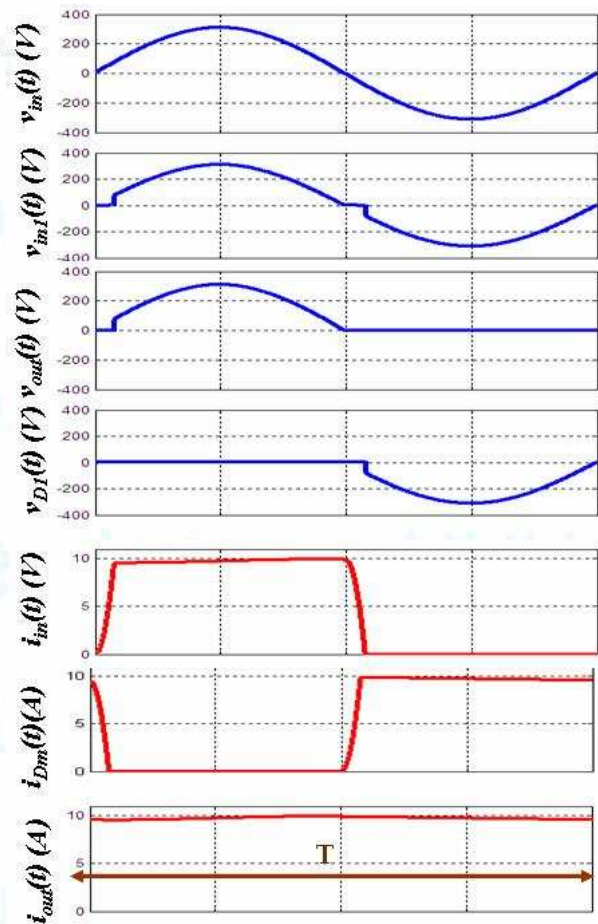
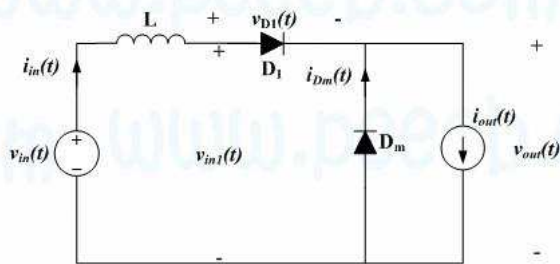
Effects of line impedance on output voltage



Presenter: Dr. Firuz Zare

www.peeeb.com

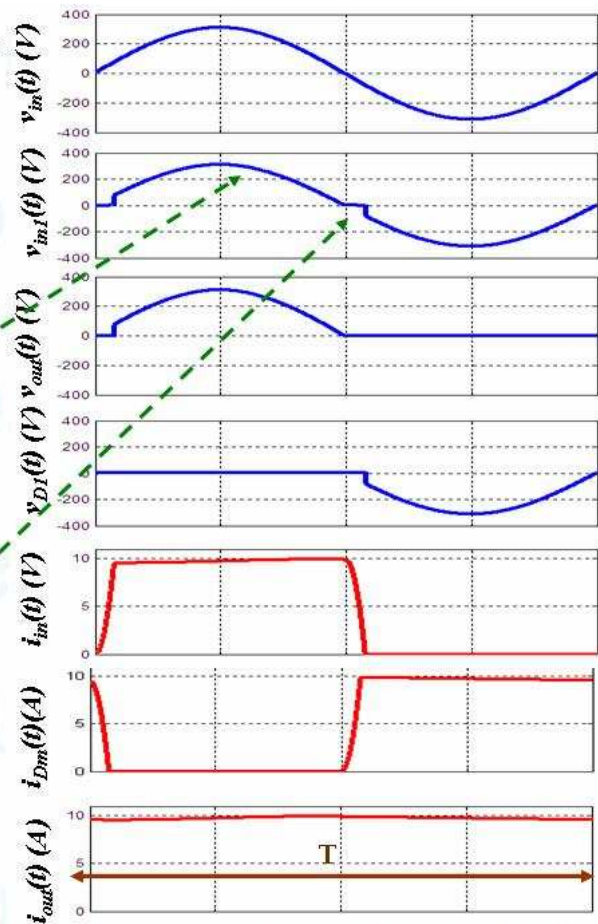
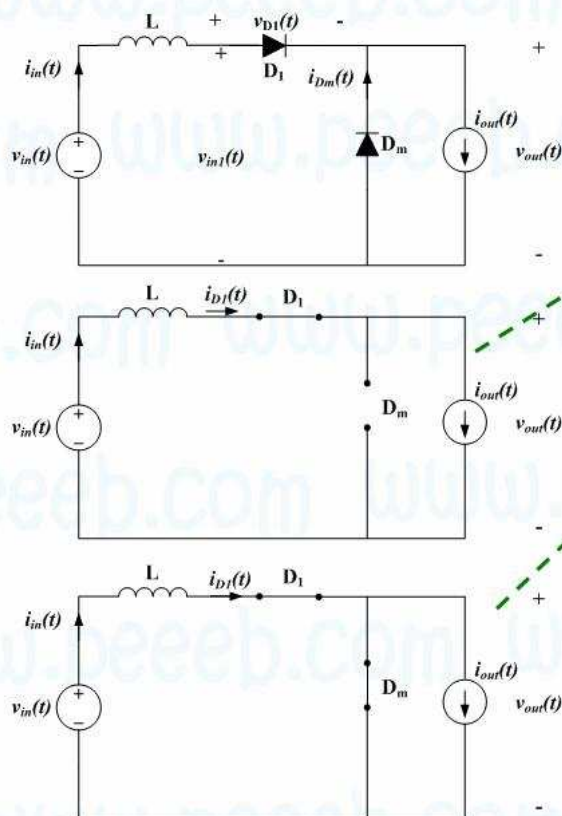
Effects of line impedance on output voltage



Presenter: Dr. Firuz Zare

www.pceeb.com

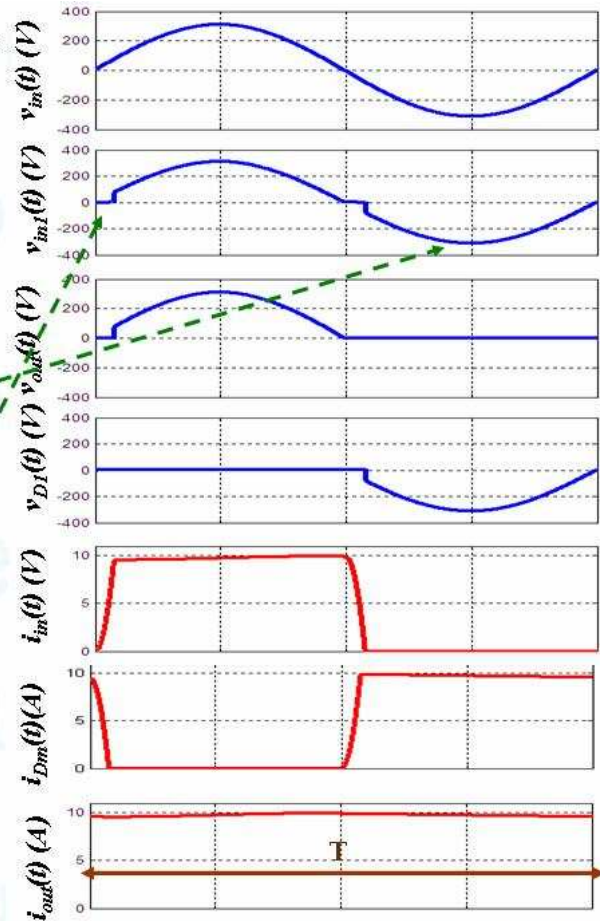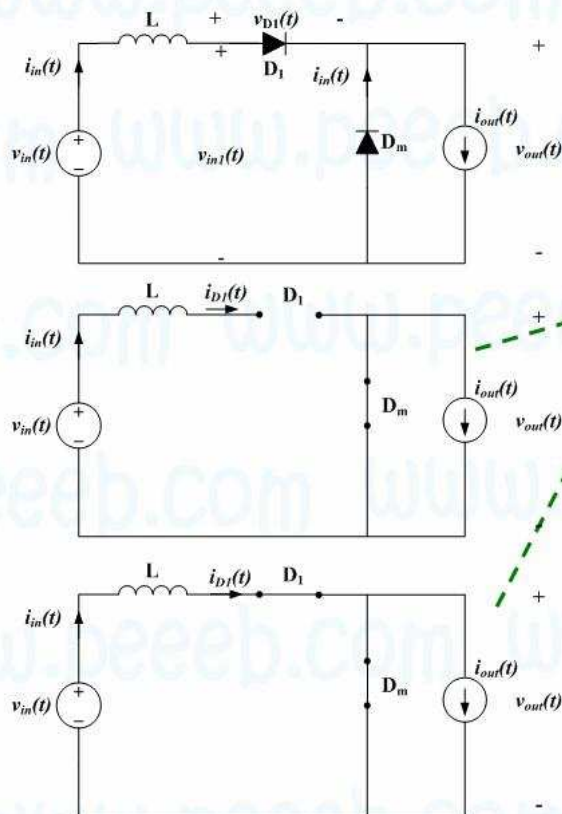Effects of line impedance on output voltage



Presenter: Dr. Firuz Zare

www.peeeb.com

Effects of line impedance on output voltage

$$L \frac{di_L(t)}{dt} = v_L(t) = V_m \sin\left(\frac{2\pi t}{T}\right)$$

$$di_L(t) = \frac{V_m}{L} \sin\left(\frac{2\pi t}{T}\right) dt$$




$$\int_0^t di_L(t) dt = \frac{V_m}{L} \int_0^{t_1} \sin\left(\frac{2\pi t}{T}\right) dt$$

$$I = \frac{V_m}{L} \left(\frac{T}{2\pi} \right) \left[-\cos\left(\frac{2\pi t}{T}\right) \right]_0^{t_1}$$

$$I = \frac{V_m T}{2\pi L} \left[-\cos\left(\frac{2\pi t_1}{T}\right) + 1 \right]$$

$$\frac{2\pi L I}{V_m T} = 1 - \cos\left(\frac{2\pi t_1}{T}\right)$$
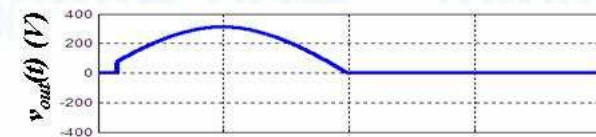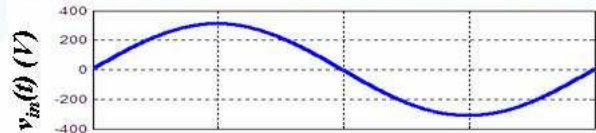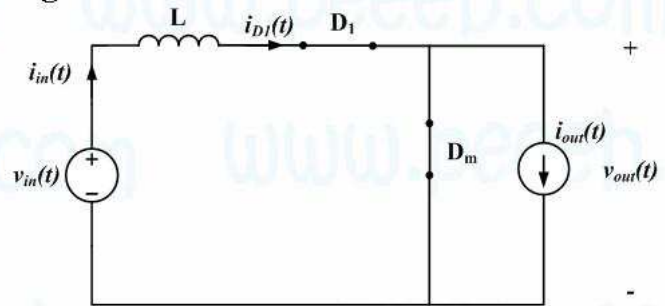
$$\cos\left(\frac{2\pi t_1}{T}\right) = 1 - \frac{2\pi L I}{V_m T}$$



Presenter: Dr. Firuz Zare

www.peeeb.com

Effects of line impedance on output voltage

$$V_{out} = \frac{1}{T} \int_0^T v_{out}(t) dt$$

$$= \frac{1}{T} \int_{t_1}^T V_m \sin\left(\frac{2\pi t}{T}\right) dt$$


$$= \frac{V_m}{T} \left(\frac{T}{2\pi}\right) \left[-\cos\left(\frac{2\pi t}{T}\right) \right]_{t_1}^T$$

$$= \frac{V_m}{2\pi} \left[-\cos(\pi) + \cos\left(\frac{2\pi t_1}{T}\right) \right]$$

$$= \frac{V_m}{2\pi} \left[1 + \cos\left(\frac{2\pi t_1}{T}\right) \right] \quad \cos\left(\frac{2\pi t_1}{T}\right) = 1 - \frac{2\pi LI}{V_m T}$$

$$= \frac{V_m}{2\pi} \left[1 + 1 - \frac{2\pi LI}{V_m T} \right]$$


$$= \frac{V_m}{\pi} - \frac{LI}{T}$$

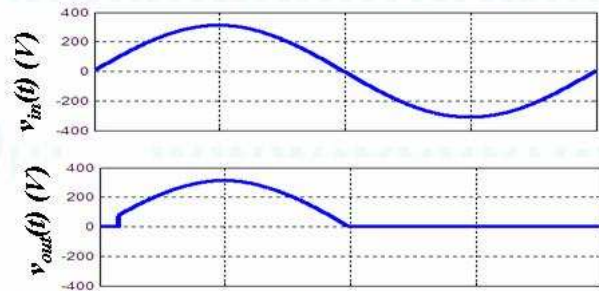


Presenter: Dr. Firuz Zare

www.peeeb.com

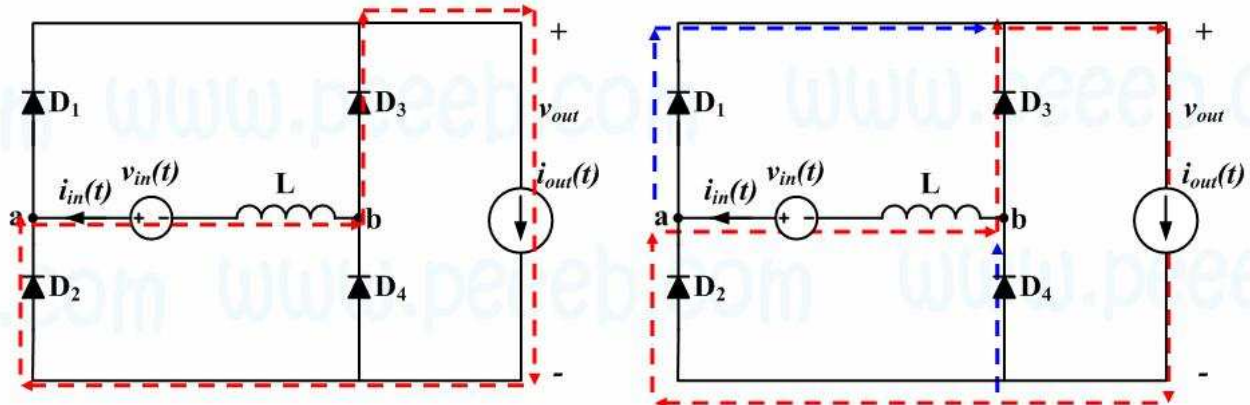Effects of line impedance on output voltage in a single phase full-wave rectifier



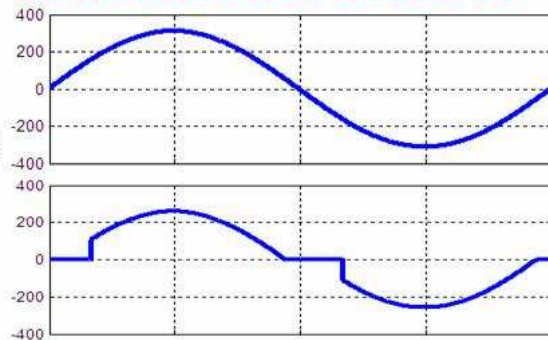
When the input voltage has gone positive, the voltage across D_1 and D_2 are positive and they are forward biased. There are short circuits in the upper loop (D_1 , D_2 and input supply) and the lower loop (D_3 , D_4 and the input supply). The diode currents (D_2 and D_3) are commutated to the other legs (D_1 and D_4).



Presenter: Dr. Firuz Zare

www.peeepb.com

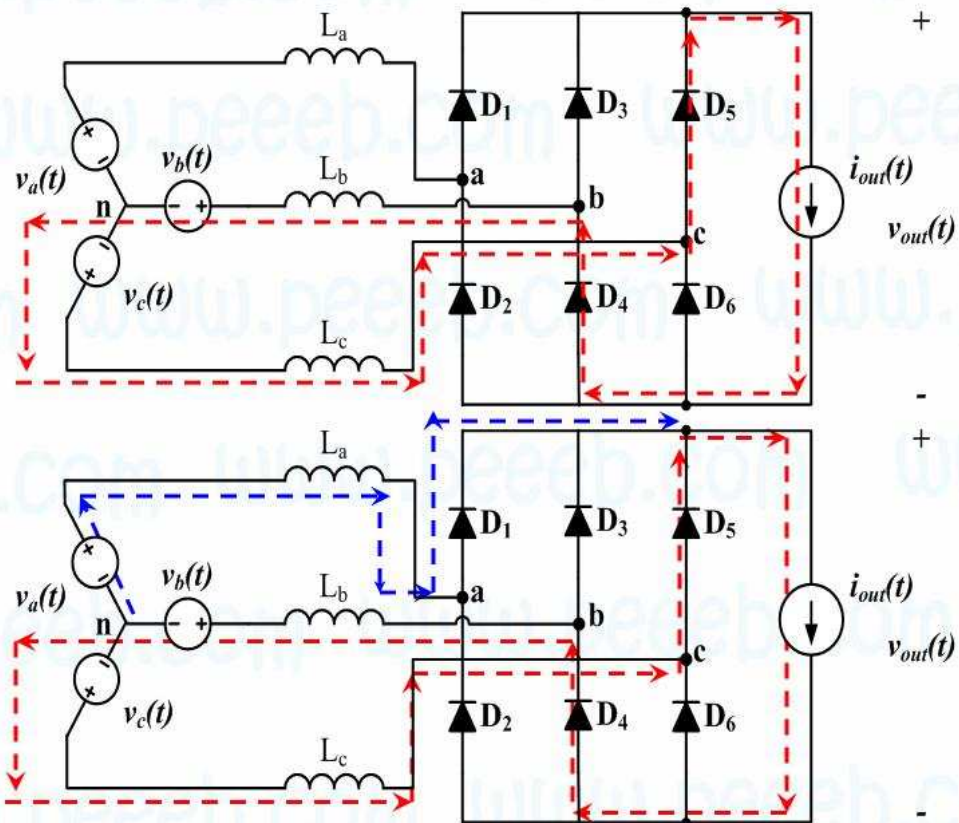
Effects of line impedance on output voltage in a three-phase full-wave rectifier



Presenter: Dr. Firuz Zare

www.peeeeb.com


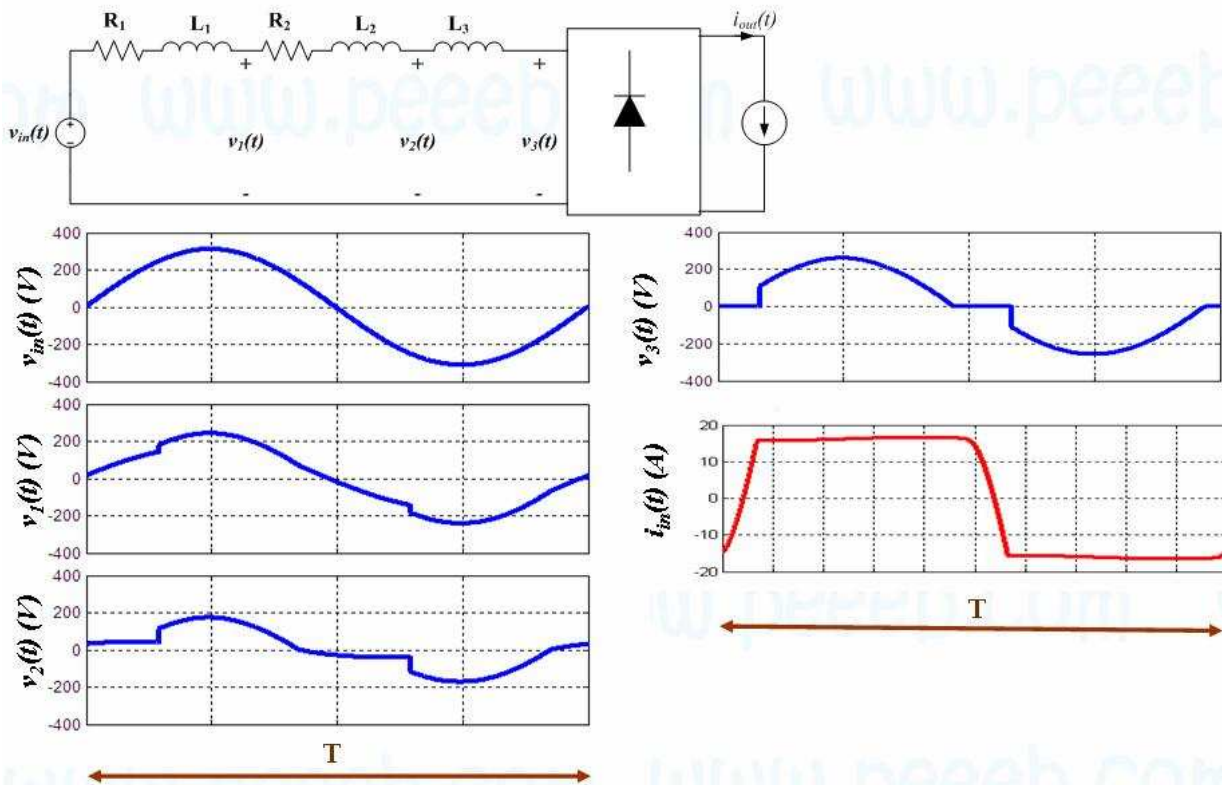
How a diode rectifier with an inductive load affects other loads in a network




Presenter: Dr. Firuz Zare

www.peeeb.com

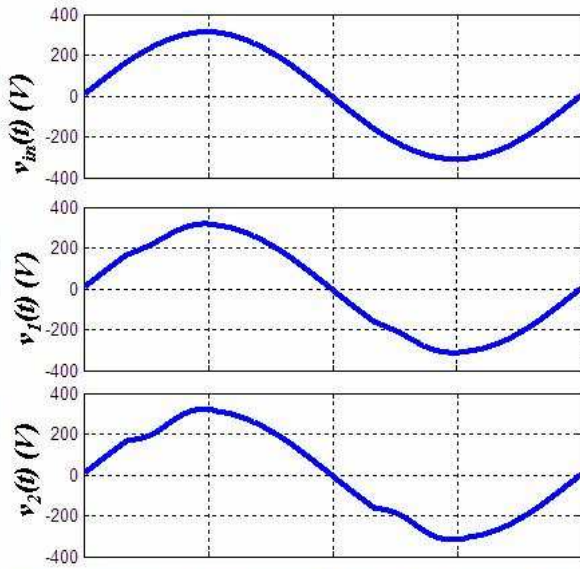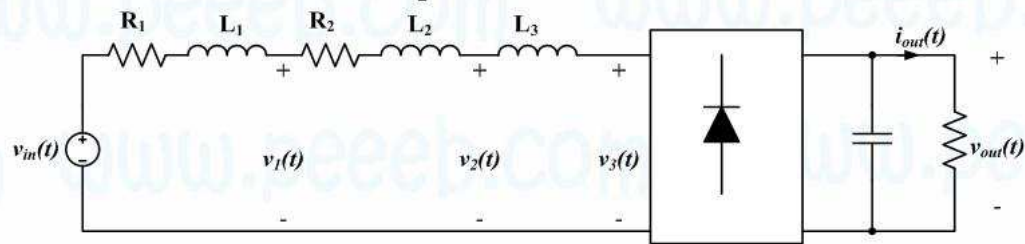How a diode rectifier with capacitive load affects other loads in a network



Presenter: Dr. Firuz Zare

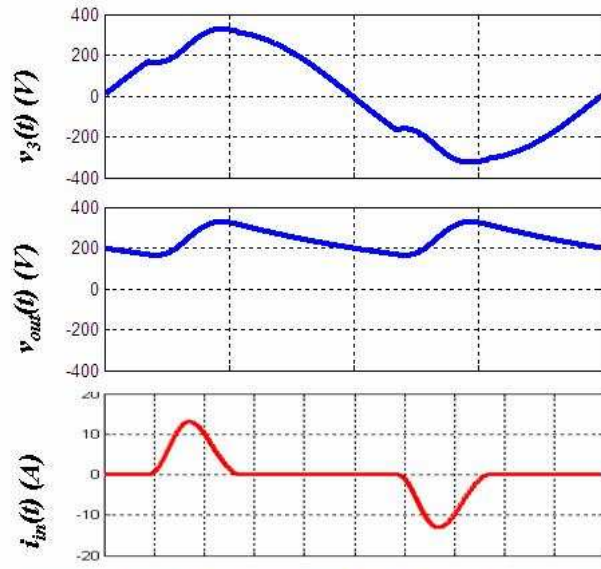

$i_{in}(t)$ (A)

T www.peeeb.com